

Белорусский государственный университет
информатики и радиоэлектроники

4-ый курс специальности ПОИТ

ПРОГРАММНОЕ ОБЕСПЕЧЕНИЕ ЦИФРОВОГО ПРОЕКТИРОВАНИЯ



2020

Introducing to VHDL

Structural Descriptions:

-- 2-inputs AND gate

Entity AND2 is

Port(

A: **in** std_logic;

B: **in** std_logic;

Z: **out** std_logic

);

End AND2;

Architecture Behavior of AND2 is
Begin

Z<=A and B;

End Behavior;

-- 3-inputs AND gate

Entity AND3 is

Port(

A,B,C : **in** std_logic;

Z : **out** std_logic

);

End AND3;

Architecture Behavior of AND3 is
Component AND2

Port(

A,B : **in** std_logic;

Z : **out** std_logic

);

End Component;


Begin

...

End Behavior;

Introducing to VHDL

Structural Descriptions:

 


Architecture Behavior of AND3 is
Component AND2

```
Port(  
  A,B   : in std_logic;  
  Z      : out std_logic  
);  
signal X: std_logic;  
End Component;  
Begin  
  -- named port mapping  
  U1: AND2 port map (A=>A, B=>B, Z=>X);  
  U2: AND2 port map (A=>X, B=>C, Z=>Z);  
  
  -- unnamed port mapping  
  -- U1: AND2 port map (A, B, X);  
  -- U2: AND2 port map (X, C, Z);  
End Behavior;
```

Introducing to VHDL

Structural Descriptions:

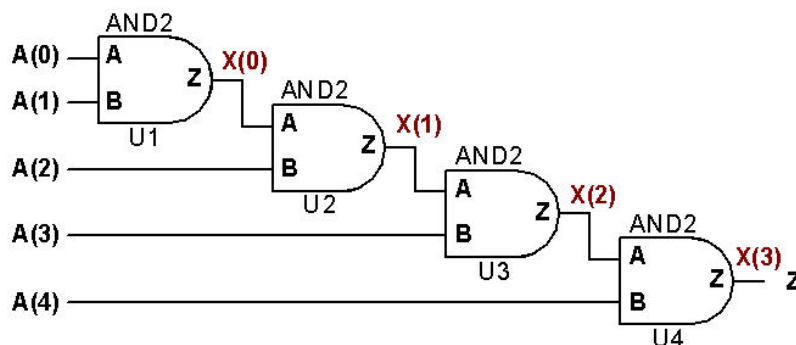

-- 5-inputs AND gate

Entity AND5 is

```
Port(  
  A      : in   std_logic_vector(4 downto 0);  
  Z      : out  std_logic  
);  
End AND5;
```

Architecture Behavior of AND5 is

Component AND2

```
Port(  
  A,B    : in  std_logic;  
  Z      : out std_logic  
);
```

End Component;

signal X: std_logic_vector(3 downto 0);

Begin

```
GEN_0: AND2 port map (A(0),A(1),X(0));
```

```
SCH: FOR J in 1 to 3 GENERATE
```

```
  GEN_J: AND2 port map (X(J-1),A(J+1),X(J));
```

```
End GENERATE;
```

```
Z<=X(3);
```

End Behavior;

Introducing to VHDL

Structural Descriptions:

-- N-inputs AND gate

Entity ANDN is

Generic (N: integer:=10);

Port(

 A : in std_logic_vector(N-1 downto 0);

 Z : out std_logic

);

End ANDN;

Architecture Behavior of ANDN is

Component AND2

Port(

 A,B : in std_logic;

 Z : out std_logic

);

End Component;

 signal X: std_logic_vector(N-2 downto 0);

Begin

 GEN_0: AND2 port map (A(0),A(1),X(0));

 SCH: **FOR** J in 1 to N-2 **GENERATE**

 GEN_J: AND2 port map (X(J-1),A(J+1),X(J));


End GENERATE;

 Z<=X(N-2);

End Behavior;

Introducing to VHDL

Behavioral Descriptions (processes):

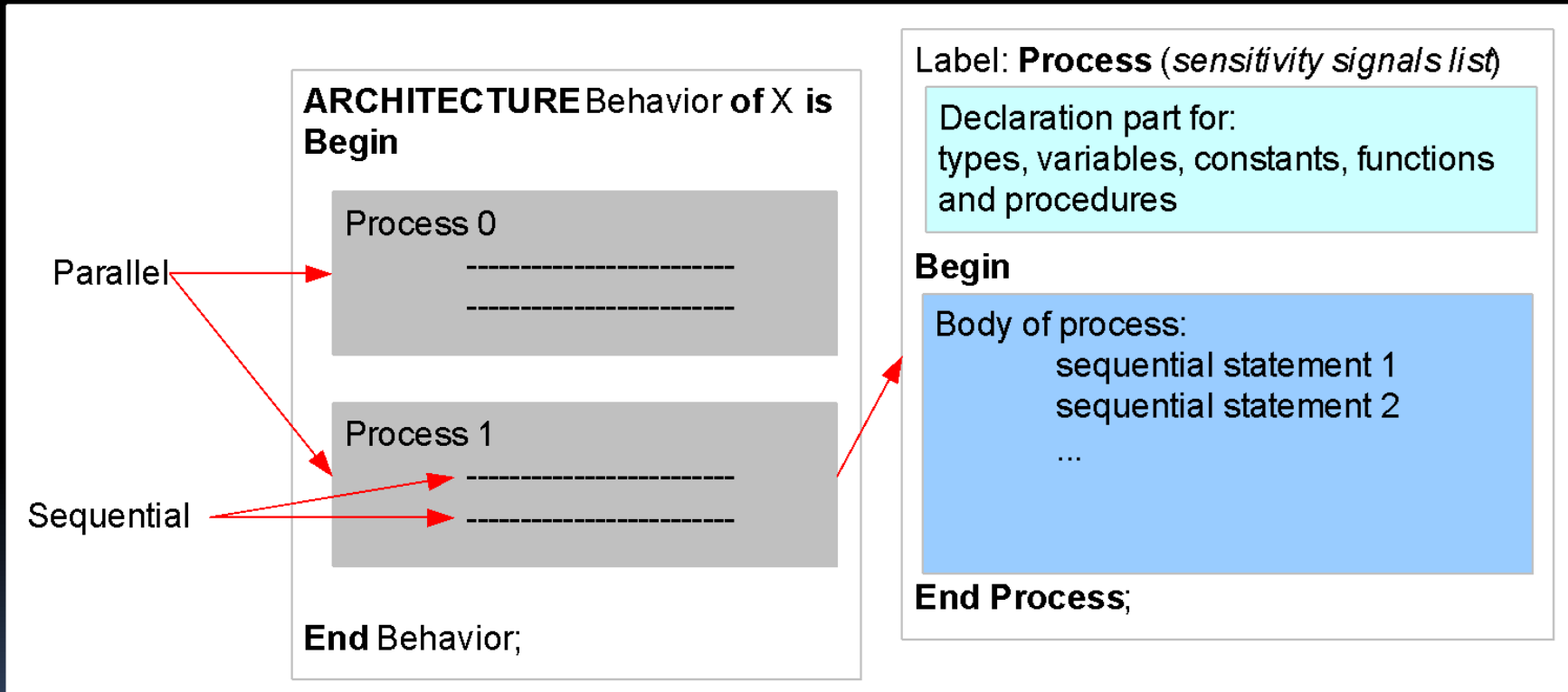

Introducing to VHDL

Behavioral Descriptions (processes):

Sensitivity list: each process can be in two states:

1. **Running** (executing sequential statements)
2. **Suspending** (waiting for signals changing).

At the beginning process is suspended. If one of the signals from sensitivity list was changed process begins to execute all sequential statements inside its body. After the last statement was executed process returns to the suspended state.

ENTITY AND2 IS

port(

A,B: in std_logic;

Z: out std_logic

);

END AND2;

--

**ARCHITECTURE Behavior OF AND2 IS
BEGIN**


Main: **process**(A,B)

begin

Z<=A and B;

end process;

END Behavior;

 

Main: **process**(A)
begin
Z<=A and B;
end process;

Error! Signal B is not in sensitivity list!

Main: **process**
begin
Z<=A and B;
end process;

Infinitive loop! Process has no wait statement

Introducing to VHDL

Behavioral Descriptions (processes):

```
ENTITY AND3 IS
  port(
    A,B,C: in std_logic;
    Z: out std_logic
  );
END AND3;

--
ARCHITECTURE Behavior OF AND3 IS
BEGIN
  Main: process(A,B,C)
    variable X: std_logic;
    begin
      X:=A and B;
      Z<=X and C;
    end process;
END Behavior;
```


At this example two statements inside process will be sequentially simulated.

1. Process Main is in suspended state.
2. One of the signals A,B or C was changed.
3. Process recognized this change by sensitivity list and starts to execute sequential statements.
4. At first the value of variable X will be calculated $X:=A$ and B.
5. Process stops until next changing of signals and Z will get a new value $Z<=X$ and C;.

The simulation of these steps will be done in Zero simulation time!

Introducing to VHDL

Combinational Logic Description:

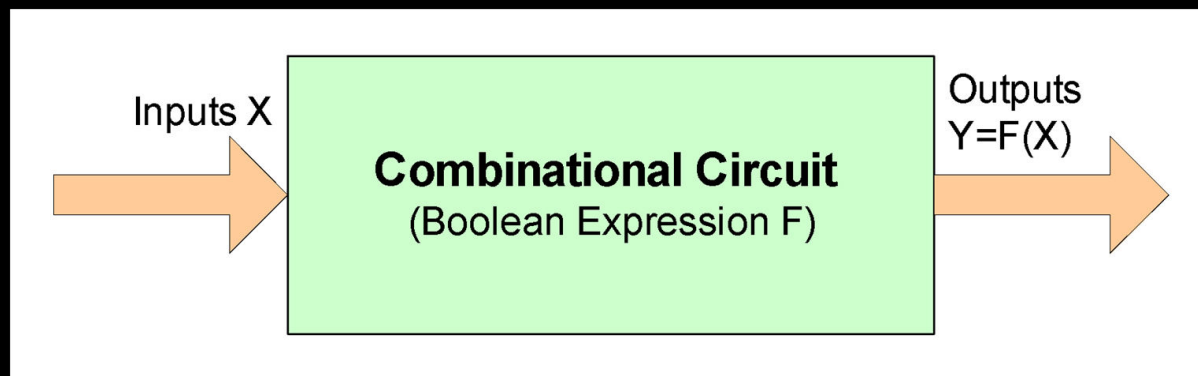

Combinational circuits can be described as behavioral and structural VHDL descriptions:

- Truth Table;
- Logic (Boolean) expression;
- Net of basic logic elements;
- High level operators and statements;


Introducing to VHDL

Combinational Logic Description:

Отрицание

a	$f(a) = \bar{a}$
0	1
1	0


Инвертор
(NOT)

 

Конъюнкция

a	b	$f(a,b) = a*b$
0	0	0
0	1	0
1	0	0
1	1	1


Двухходовой
вентиль И
(AND)

 

Дизъюнкция

a	b	$f(a,b) = a+b$
0	0	0
0	1	1
1	0	1
1	1	1

Двухходовой
вентиль ИЛИ
(OR)

 

Introducing to VHDL


Combinational Logic Description:

Таблица истинности
и минтермы функции $f(a,b,c)$

a	b	c	Минтермы	$f(a,b,c)$
0	0	0	$m_0 = \bar{a} \cdot \bar{b} \cdot \bar{c}$	$f_0 = 0$
0	0	1	$m_1 = \bar{a} \cdot \bar{b} \cdot c$	$f_1 = 1$
0	1	0	$m_2 = \bar{a} \cdot b \cdot \bar{c}$	$f_2 = 1$
0	1	1	$m_3 = \bar{a} \cdot b \cdot c$	$f_3 = 0$
1	0	0	$m_4 = a \cdot \bar{b} \cdot \bar{c}$	$f_4 = 1$
1	0	1	$m_5 = a \cdot \bar{b} \cdot c$	$f_5 = 0$
1	1	0	$m_6 = a \cdot b \cdot \bar{c}$	$f_6 = 0$
1	1	1	$m_7 = a \cdot b \cdot c$	$f_7 = 1$

$$f(a,b,c) = f_1 \cdot m_1 + f_2 \cdot m_2 + f_4 \cdot m_4 + f_7 \cdot m_7.$$

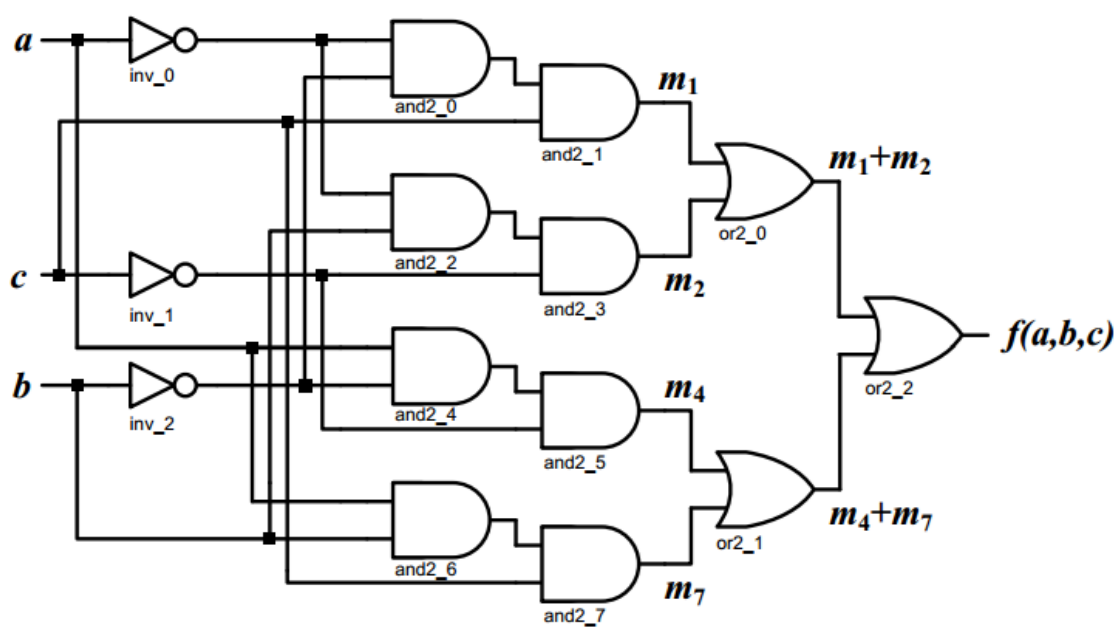
$$f(a,b,c) = \bar{a} \cdot \bar{b} \cdot c + \bar{a} \cdot b \cdot \bar{c} + a \cdot \bar{b} \cdot \bar{c} + a \cdot b \cdot c.$$




Introducing to VHDL

Combinational Logic Description:

Result of RTL-synthesis

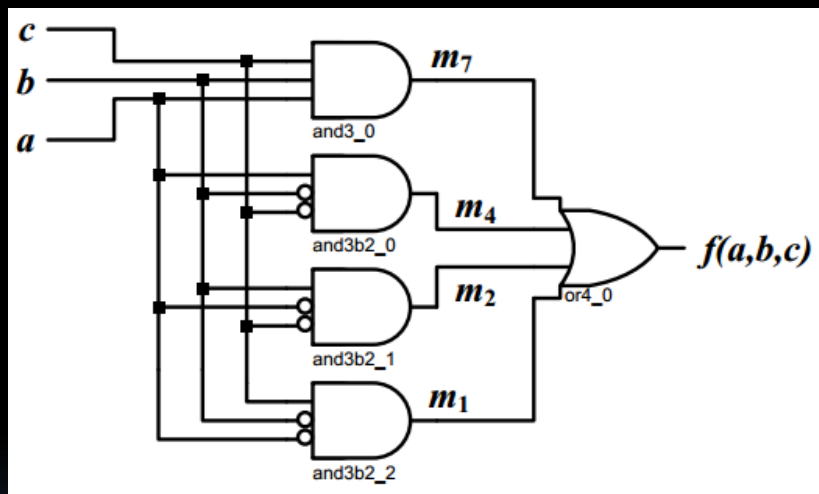

Result of FPGA implementation

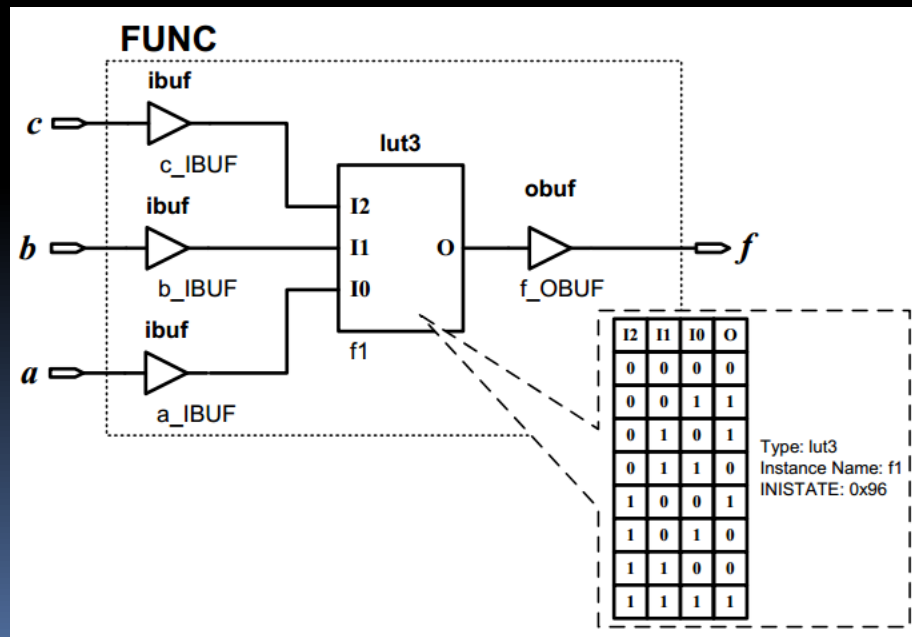

Introducing to VHDL

Combinational Logic Description:

VHDL description #1

```
-- ...  
signal m1, m2, m4, m7 : std_logic;  
-- ...  
      m1 <= (not a) and (not b) and c;  
      m2 <= (not a) and b and (not c);  
      m4 <= a and (not b) and (not c);  
      m7 <= a and b and c;  
      f  <= m1 or m2 or m4 or m7;  
-- ...
```

VHDL description #2

```
-- ...  
P0: process( a, b, c )  
  variable m1, m2, m4, m7 : std_logic;  
  -- ...  
  begin  
      m1 := (not a) and (not b) and c;  
      m2 := (not a) and b and (not c);  
      m4 := a and (not b) and (not c);  
      m7 := a and b and c;  
      f  <= m1 or m2 or m4 or m7;  
  end process;  
-- ...
```

Introducing to VHDL

Combinational Logic Description:

VHDL description #3 :-)

```
-- ...  
      f <= a xor b xor c;  
-- ...
```

VHDL description #4 **with-select** parallel operator

```
-- ...  
signal abc: std_logic_vector(2 downto 0);  
-- ...  
      abc <= a & b & c;  
      with abc select  
      f <= '1' when "001" | "010" | "100" | "111",  
          '0' when others;  
-- ...
```

Introducing to VHDL

Combinational Logic Description:

VHDL description #5 **case** sequential operator

```
-- ...
P0: process ( a, b, c )
  variable abc: std_logic_vector(2 downto 0);
-- ...
begin
  abc := a & b & c;
  case abc is
    when "001" | "010" | "100" | "111" =>
      f <= '1';
    when others => f <= '0';
  end case;
end process;
-- ...
```

Combinational Circuit Description needs complete logic statements
(all variants of assigned values)

Introducing to VHDL

Combinational Logic Description:

$$f(a, b, s) = a \cdot \bar{s} + b \cdot s$$

```
-- ...  
P0: process ( a, b, s )  
begin  
    if s = '0' then  
        f <= a;  
    else  
        f <= b;  
    end if;  
end process;  
-- ...
```

?

```
-- ...  
P0: process ( a, b, s )  
begin  
    if s = '0' then  
        f <= a;  
    else  
        f <= 'Z';  
    end if;  
end process;  
-- ...
```

?

```
-- ...  
P0: process ( a, b, s )  
begin  
    if s = '0' then  
        f <= a;  
    end if;  
end process;  
-- ...
```

?

Introducing to VHDL

Combinational Logic Description:

$$f(a, b, c, s(1), s(0)) = a \cdot \overline{s(1)} \cdot \overline{s(0)} + b \cdot \overline{s(1)} \cdot s(0) + c \cdot s(1) \cdot \overline{s(0)}.$$

```
-- ...
P0: process ( a, b, c, s )
begin
    if s="00" then
        f <= a;
    elsif s="01" then
        f <= b;
    elsif s="10" then
        f <= c;
    end if;
end process;
-- ...
```

Where is a mistake?


a,b,c,s,f – are signals (ports)

Introducing to VHDL

Combinational Logic Description:

```
— ...
P0: process ( a, b, c, s )
begin
    if s="00" then
        f <= a;
    elsif s="01" then
        f <= b;
    elsif s="10" then
        f <= c;
    end if;
end process;
— ...
```

Behavioral Description

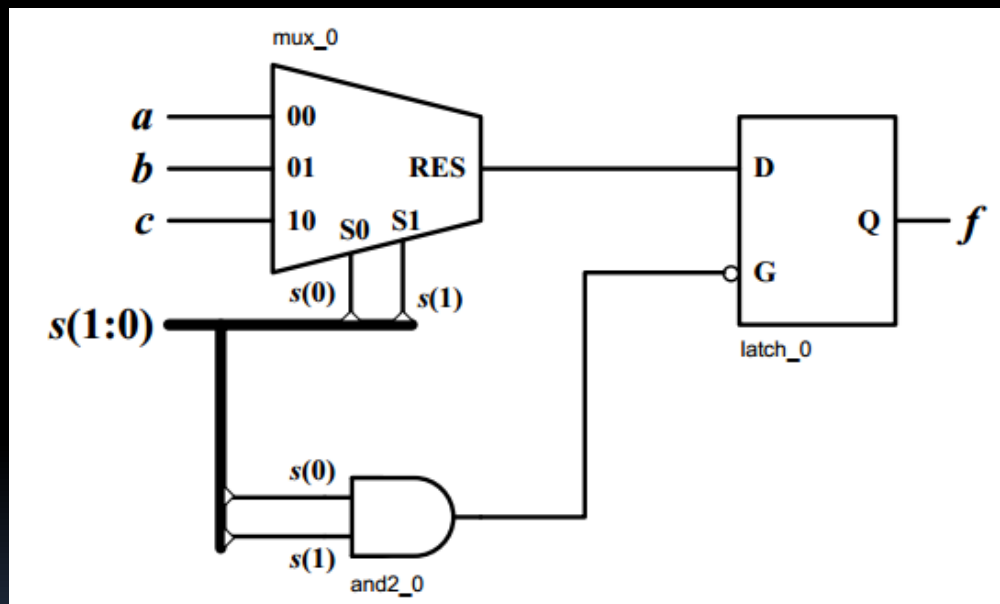


Result of RTL-synthesis

Introducing to VHDL

Combinational Logic Description:

```
-- ...  
P0: process ( a, b, c, s )  
begin  
    if s="00" then  
        f <= a;  
    elsif s="01" then  
        f <= b;  
    elsif s="10" then  
        f <= c;  
    else  
        f <= '0';  
    end if;  
end process;  
-- ...
```

Good Behavioral
Description

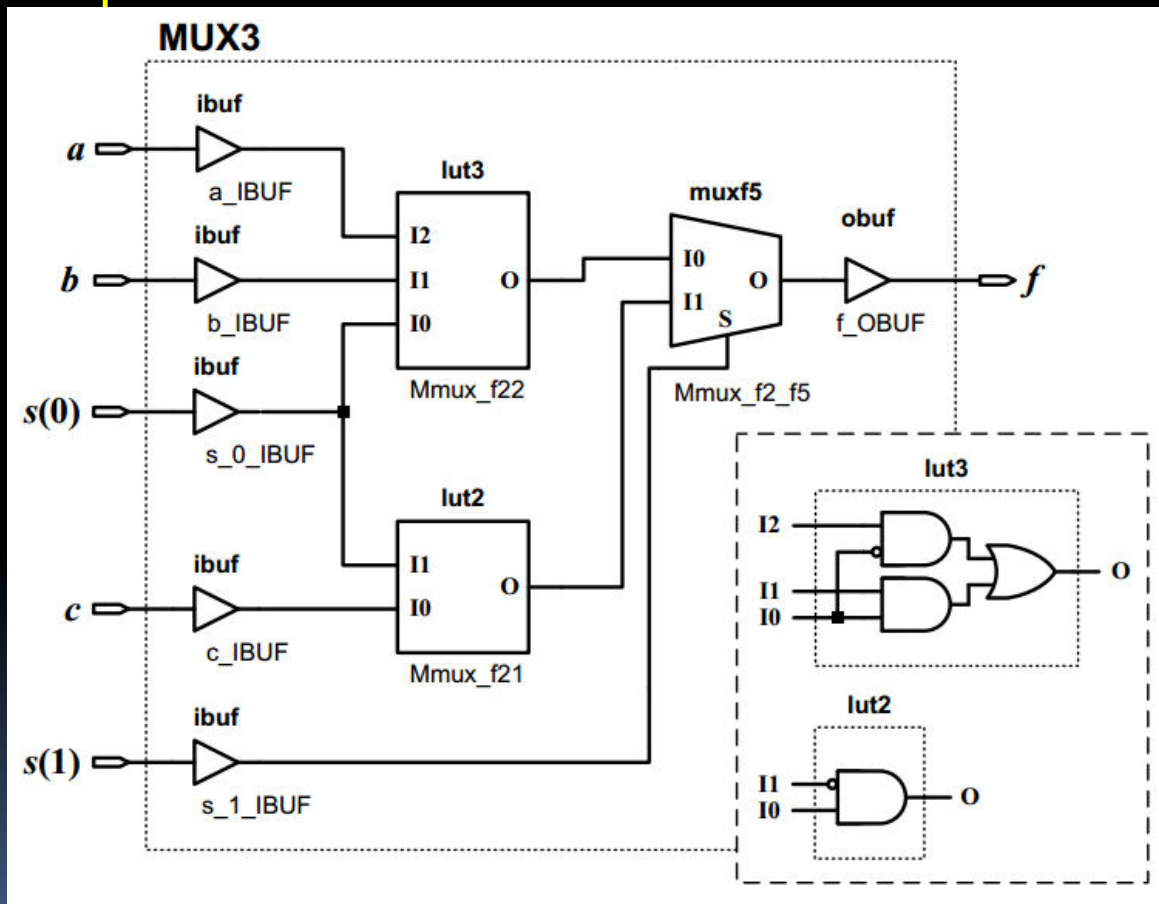

Result of Schematic Synthesis