

Белорусский государственный университет
информатики и радиоэлектроники

4-ый курс специальности ПОИТ

ПРОГРАММНОЕ ОБЕСПЕЧЕНИЕ ЦИФРОВОГО ПРОЕКТИРОВАНИЯ



2020

Introducing to VHDL

HDL – Hardware Description Language

VHDL, Verilog, SystemVerilog, SystemC, Handel-C, CUPL, AHDL, ABEL, PALASM, etc.

VHDL => VHSIC HDL, **VHSIC** => Very High Speed Integrated Circuit

ADA, Pascal-like language

U.S Department of Defense in 1980^s

IEEE Standard 1076

Introducing to VHDL

VHDL main features:

- 1) VHDL supports the whole design process:
 - System Level;
 - RT Level;
 - Circuit Level;
 - Logic gates Level;
- 2) VHDL is suitable for specification in
 - Behavioral domain;
 - Structural domain.
- 3) Precise simulation semantics is associated with the VHDL language constructs.


Introducing to VHDL

Synthesized and Not Synthesized descriptions

Behavioral Description	$Z \leq A \text{ and } B;$	Synthesized description, which uses signals, built-in logic operators, processes as a sequential subroutines and at the same time process can be a description for sequential circuit.
Structural Description	U1: AND_GATE port map (A,B,Z)	Synthesized description, which describes the digital system as a set of components and the interconnections between these components.
Time Description	$Z \leq A \text{ and } B \text{ after } 10 \text{ ns};$	Not Synthesized description, which describes the behavior of the digital system in time using gates delay slots and signals transportation time.
Mixed Description	Component description as $Z \leq A \text{ and } B.$	Can be both: synthesized and not synthesized description. Simultaneously uses several types of HDL description.


Introducing to VHDL

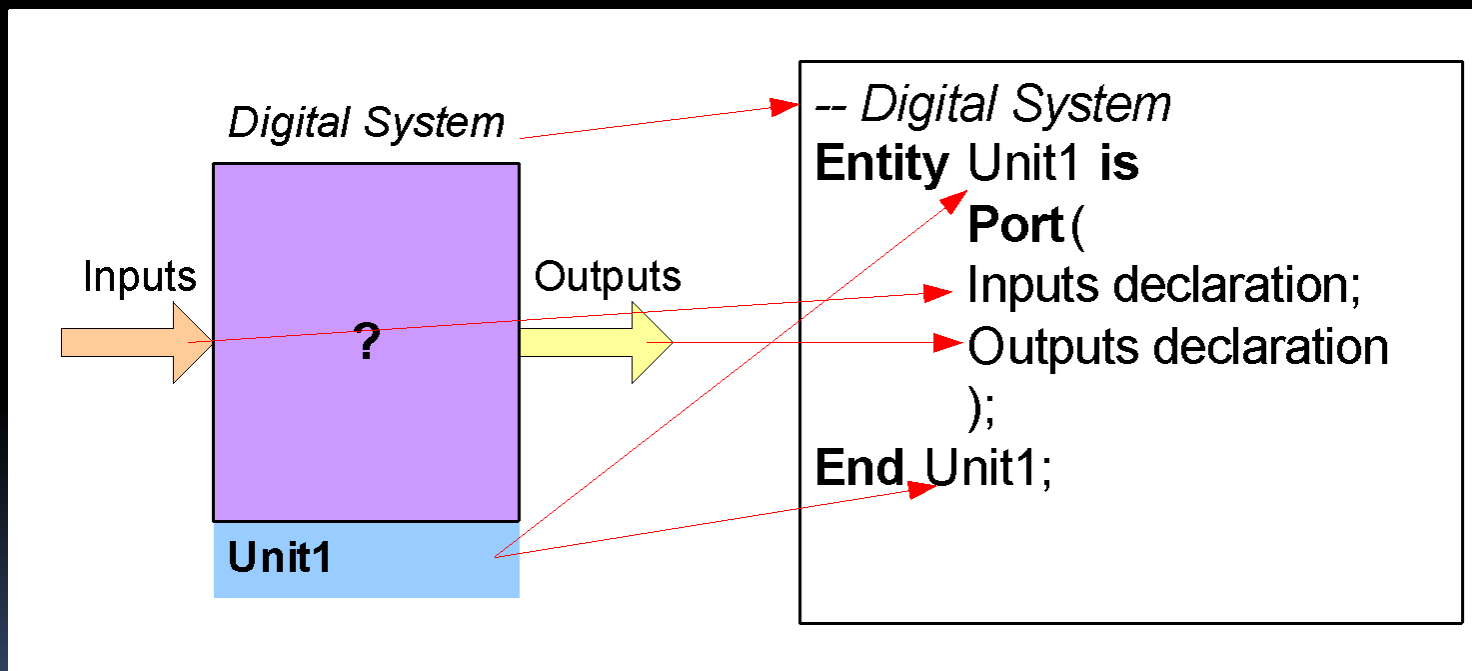VHDL operates with **COMPONENTS**. Each COMPONENT has its own **ENTITY** and **ARCHITECTURE**.



Introducing to VHDL

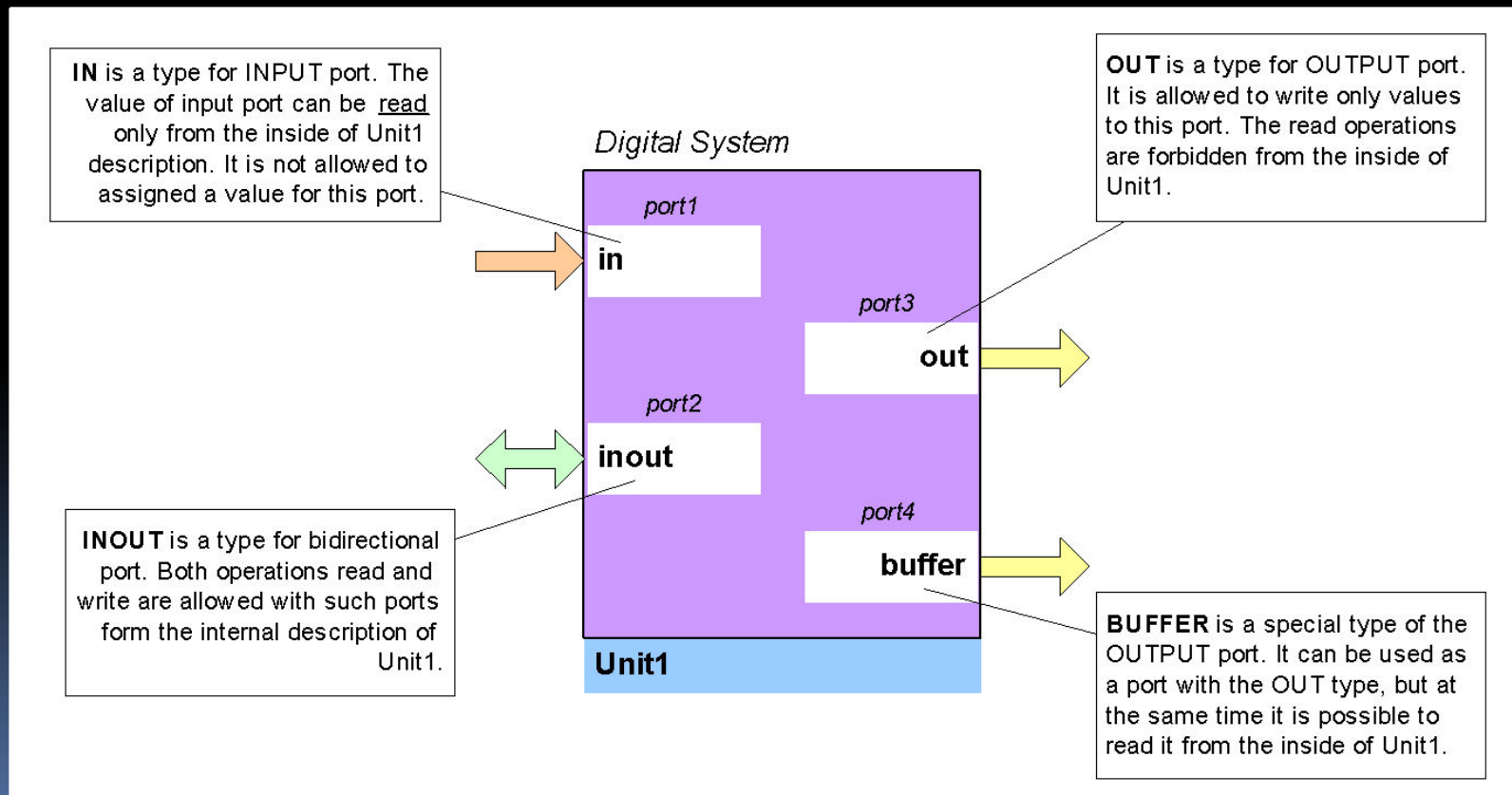Ports: port is an object, which is used to provide the connection between the internal structure of the component and external environment.



Introducing to VHDL

Ports declaration : each port should have a type of a signal. There are several signal types in VHDL, but most important is **STD_LOGIC** type. Any object of this type can assume next values:


- 'U' – Uninitialized value;
- 'X' – Forcing unknown;
- '0' – Forcing 0;
- '1' – Forcing 1;
- 'Z' – High impedance;
- 'W' – Weak unknown;
- 'L' – Weak 0;
- 'H' – Weak 1;
- '-' – Don't care.

Another example is **BIT** type, which uses only two values:

- '0' – Logic 0;
- '1' – Logic 1.


Introducing to VHDL

Ports declaration:

 

```
-- Digital System
Entity Unit1 is
  Port(
    port1: in      std_logic;
    port2: inout   std_logic;
    port3: out     std_logic;
    port4: buffer  std_logic
  );
End Unit1;
```


Example:

 

```
-- 2-inputs AND gate
Entity AND2 is
  Port(
    A: in  std_logic;
    B: in  std_logic;
    Z: out std_logic
  );
End AND2;
```


Introducing to VHDL


Ports declaration: STD_LOGIC_VECTOR type

 

```
-- Digital System
Entity Unit1 is
  Port(
    port1: in      std_logic_vector(3 downto 0);
    port2: inout   std_logic_vector(1 downto 0);
    port3: out     std_logic_vector(0 to 7);
    port4: buffer std_logic_vector(1 to 3)
  );
End Unit1;
```


- increasing numeric significance with increasing memory addresses (or increasing time), known as *little-endian*, and
- decreasing numeric significance with increasing memory addresses (or increasing time), known as *big-endian*^[note 2]

Example:

 

std_logic_vector(3 **downto** 0)

Little-endian

 


std_logic_vector(1 **to** 3)

Big-endian

Introducing to VHDL

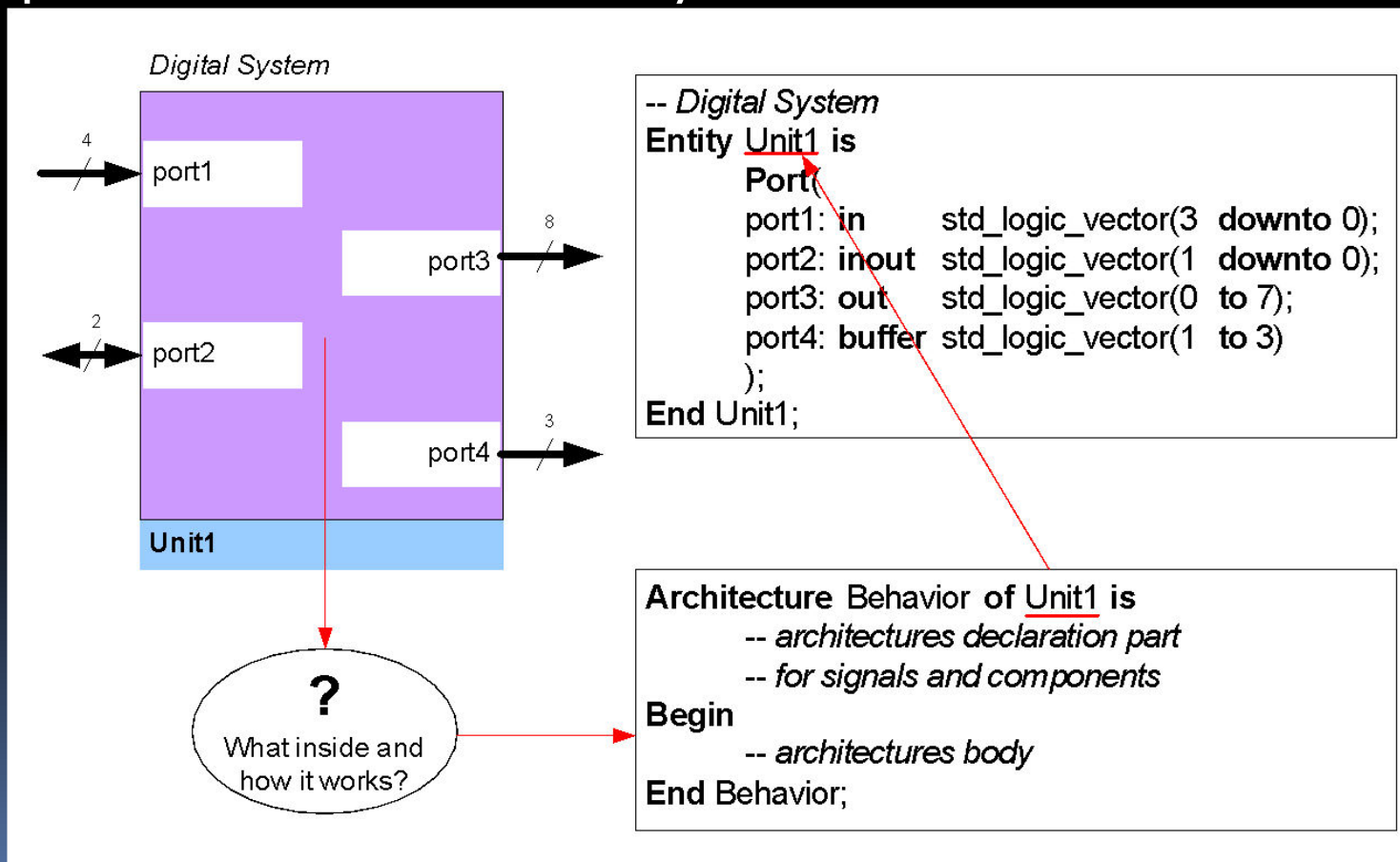
Architecture: this block of VHDL represents the description of declared entity.



Introducing to VHDL

Architecture:

Digital System

 

-- Digital System

Entity Unit2 is

Port(

-- Joint declaration, only for ports of the same type!

Out1, Out2 : out std_logic;

Out3 : out std_logic_vector(3 to 0);

Out4 : out std_logic_vector(7 to 0)

);

End Unit1;

Architecture Behavior of Unit2 is

Begin

Out1<='1';

Out2<='0';

Out3<="0011";


Out4<="11110000";

End Behavior;

Introducing to VHDL

Architecture: there are several built-in logic operators in VHDL, which can be used for ports and for signals. They are: **AND, OR, NOT, XOR, NAND, NOR, XNOR.**

Example:

 

– 2-inputs AND gate

Entity AND2 is

Port(

A: **in** std_logic;

B: **in** std_logic;

Z: **out** std_logic

);

End AND2;

Architecture Behavior of AND2 is
Begin

Z<=A and B;

End Behavior;


Introducing to VHDL

Architecture: each expression inside the architectures body is **parallel expression**.

 Example:

```
Entity X is
  Port(
    A: in  std_logic;
    B: in  std_logic;
    Z: out std_logic
  );
End X;
```

```
Architecture Behavior of X is
Begin
  Z<=A and B;
  Z<=A or B;
End Behavior;
```




Error: which value must be assigned to the output port Z?

Introducing to VHDL

Architecture: for **STD_LOGIC** type there are special rules how to simulate the situations with the multiple drivers for one port or signal. These rules are represented as the **Resolution Table** for STD_LOGIC objects:

U	X	0	1	Z	W	L	H	-
U	U	U	U	U	U	U	U	U
U	X	X	X	X	X	X	X	X
U	X	0	X	0	0	0	0	X
U	X	X	1	1	1	1	1	X
U	X	0	1	Z	W	L	H	X
U	X	0	1	W	W	W	W	X
U	X	0	1	L	W	L	W	X
U	X	0	1	H	W	W	H	X
U	X	X	X	X	X	X	X	X

 

Introducing to VHDL

Architecture: special objects – **signals**

-- 3-inputs AND gate

Entity AND3 is

Port (

A,B,C: **in** std_logic;

Z: **out** std_logic

);

End AND3;

Architecture Behavior of AND3 is


signal X: std_logic;

Begin

X<=A and B;

Z<=C and X;

End Behavior;

 


Introducing to VHDL

Architecture: signals are similar to wires (parallel objects)

```
Entity W is
  Port(
    A,B,C: in    std_logic;
    Z1,Z2: out   std_logic
  );
End W;
```
 
```
Architecture Behavior of W is
  signal X: std_logic;
Begin
  X<=A and B;
  Z1<=C and X;
  X<=A or B;
  Z2<=C or X;
End Behavior;
```



The Signal is similar to a wire